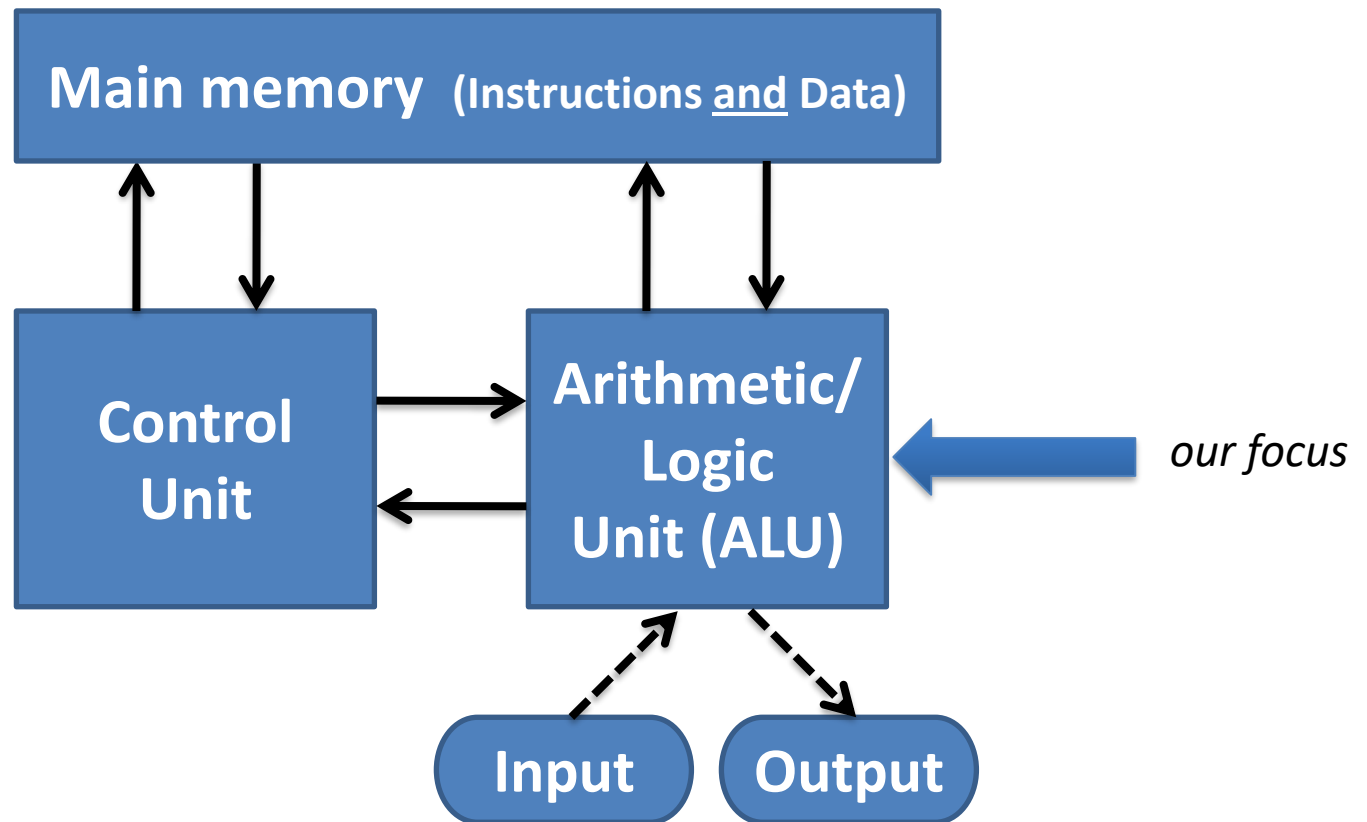


SCC131: Digital Systems

Topic 6: Building the ALU

Reminder of the von Neumann architecture




What is the role of the ALU? (1)

- Implements arithmetic and logic operations:
 - add, subtract, multiply, divide, shift of integers, ...
 - (perhaps also floating point operations; or may use a separate floating point unit (FPU))
 - and, or, not, xor, ...
 - comparisons: $<$, \leq , $=$, \neq , \geq , $>$

What is the role of the ALU? (2)

- Provides the following facilities:
 - registers: working storage for operands and results
 - status flags: typically, **overflow**, **zero** and **negative**
 - Overflow flag tells us if the previous arithmetic instruction resulted in overflow
 - Zero and negative are also set by arithmetic operations, and are typically used to determine the outcome of branch decisions

The ALU in outline

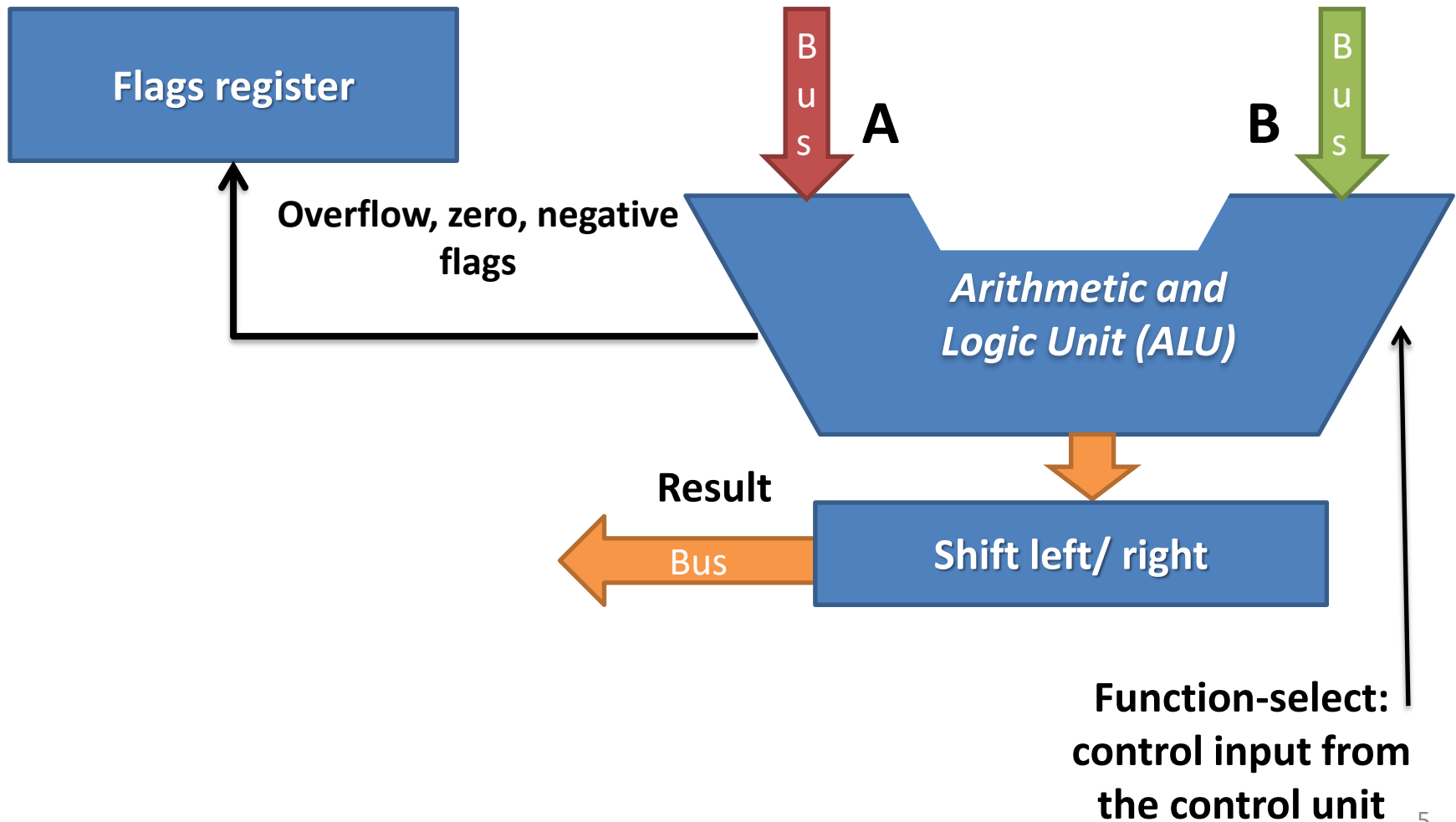

Adding two binary bits: the “half adder”

HALF ADDER

A	B	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

SUM

A	B	S
0	0	0
0	1	1
1	0	1
1	1	0

CARRY

A	B	C
0	0	0
0	1	0
1	0	0
1	1	1


Implementing a half adder

$$\text{SUM} = A \oplus B$$

A	B	Q
0	0	0
0	1	1
1	0	1
1	1	0


$$\text{CARRY} = AB$$

A	B	Q
0	0	0
0	1	0
1	0	0
1	1	1

 

We can break the \oplus down into something easier to build...

Half adder with expanded \oplus

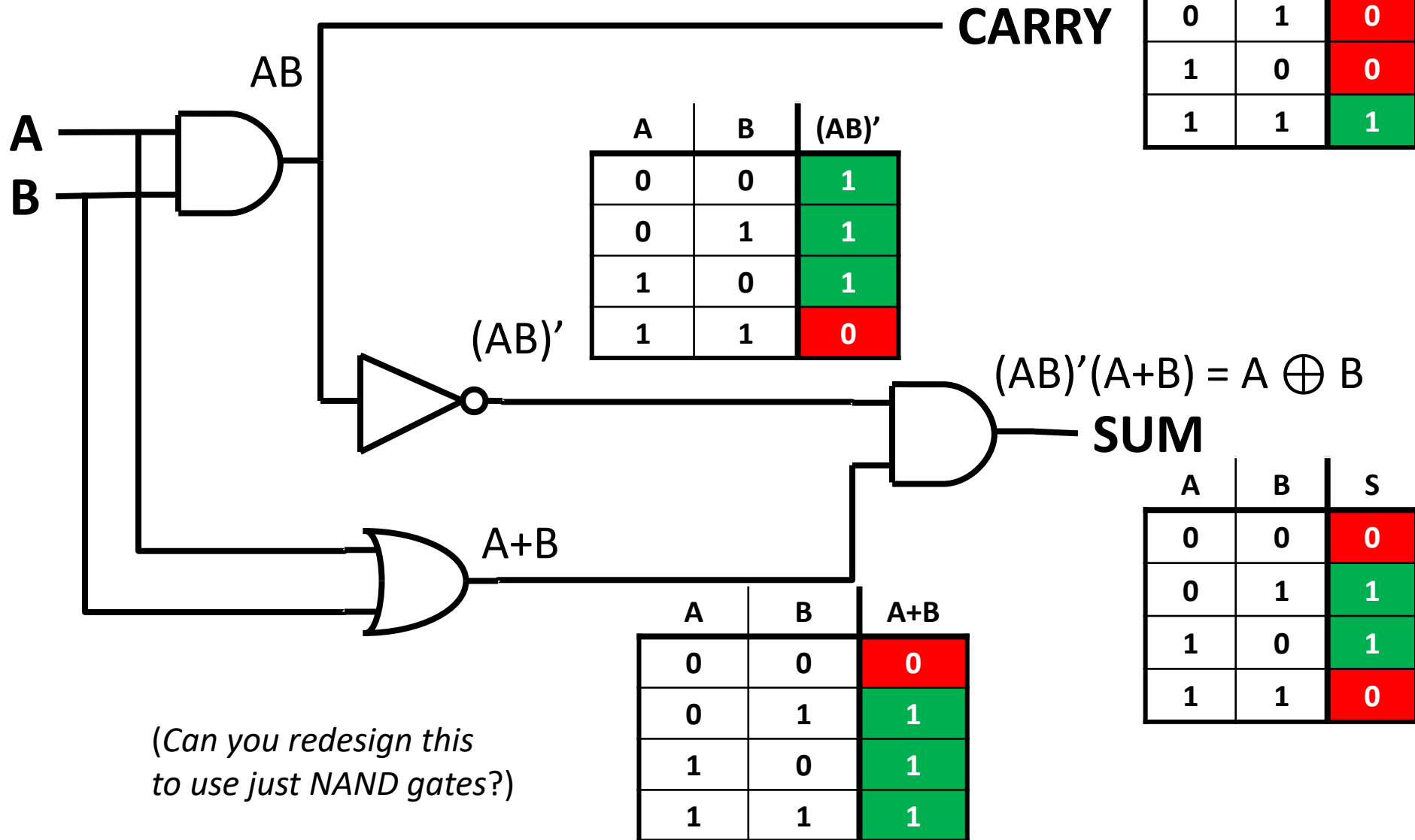


A	B	C
0	0	0
0	1	0
1	0	0
1	1	1

A	B	S
0	0	0
0	1	1
1	0	1
1	1	0

Adding the 3rd bit


- A half adder adds only *two* bits
- But when adding mult-digit numbers consisting of multiple bits, we need also to consider CARRYs
 - When CARRYs are considered, we need to be able to add **3** bits: two input bits plus a possible CARRY from the previous stage
 - Where the CARRY and input bits are all 1s, this results in a maximum output of 3 (i.e., $1 + 1 + 1 = 11$)
- To add these 3 bits, we can use *two* half adders; this is called a **full adder**...

Full adder

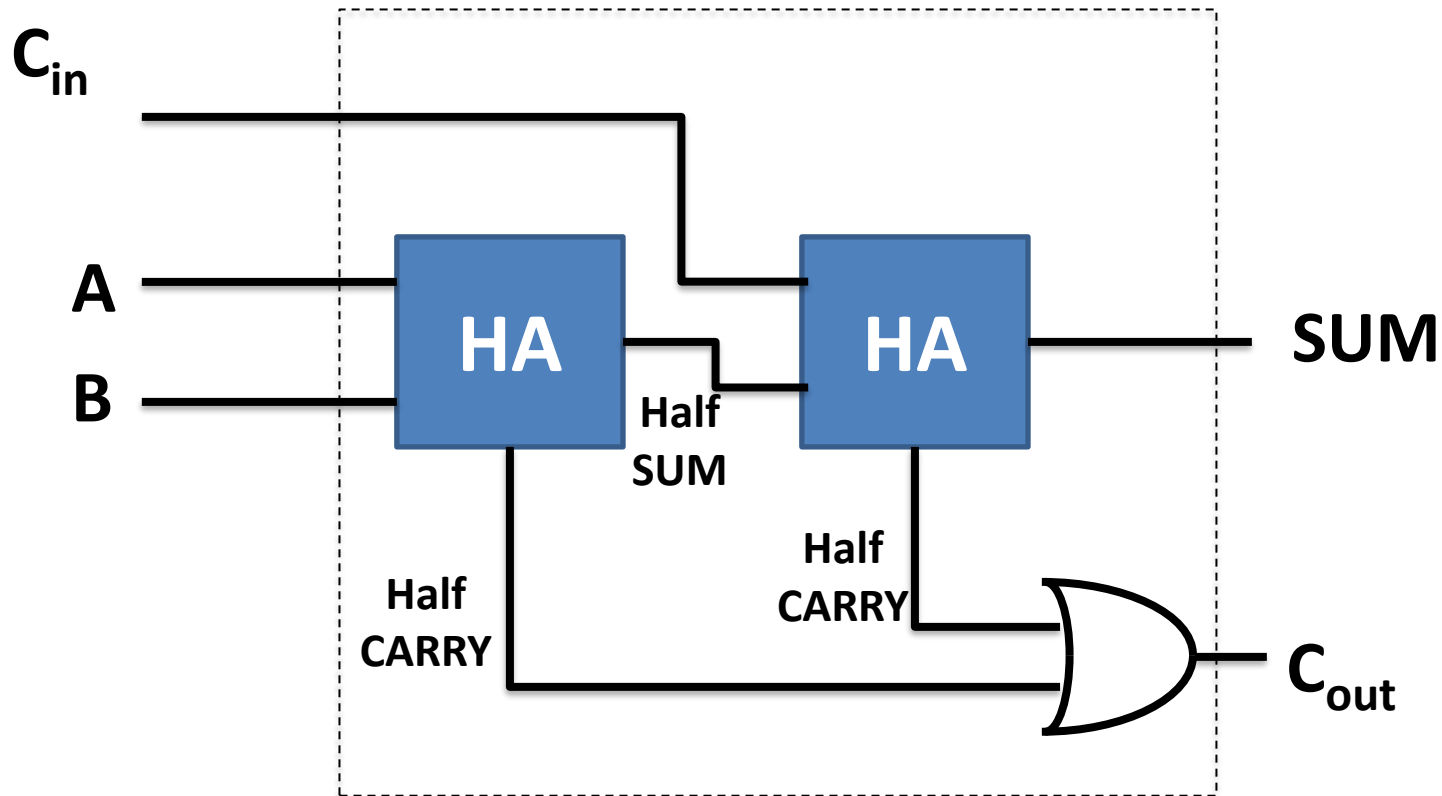

By combining these we can build adders that can handle any length of numbers...

Why does this work?

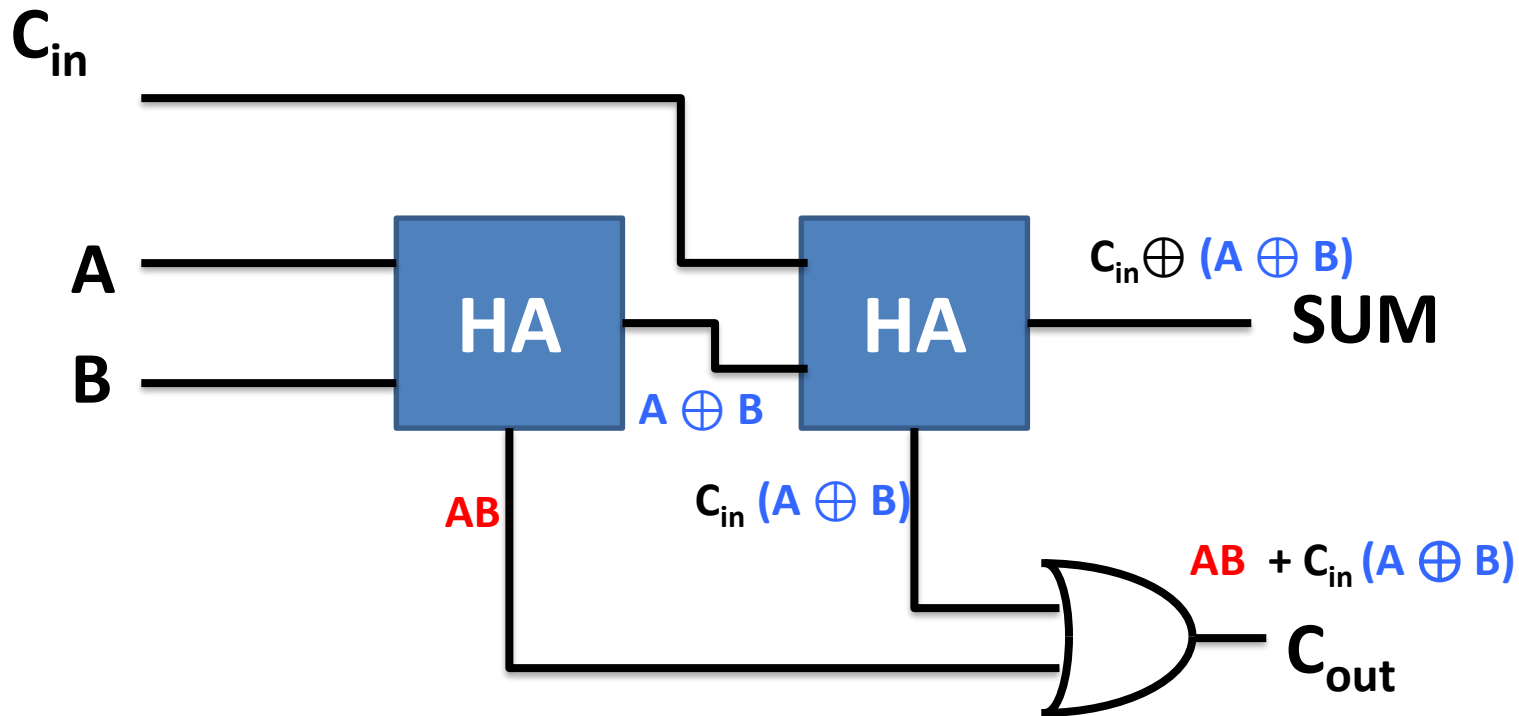

$$SUM = C_{in} \oplus (A \oplus B)$$

$$C_{out} = AB + C_{in} (A \oplus B)$$


Proof by perfect induction

C_{in}	A	B	SUM	C_{out}	$A \oplus B$	$C_{in} \oplus (A \oplus B)$	AB	$C_{in} (A \oplus B)$	$AB + C_{in} (A \oplus B)$
0	0	0	0	0	0	0	0	0	0
0	0	1	1	0	1	1	0	0	0
0	1	0	1	0	1	1	0	0	0
0	1	1	0	1	0	0	1	0	1
1	0	0	1	0	0	1	0	0	0
1	0	1	0	1	1	0	0	1	1
1	1	0	0	1	1	0	0	1	1
1	1	1	1	1	0	1	1	0	1

$$C_{out} = AB + C_{in} (A \oplus B)$$

$$SUM = C_{in} \oplus (A \oplus B)$$

Multi-stage full adder with ripple carry

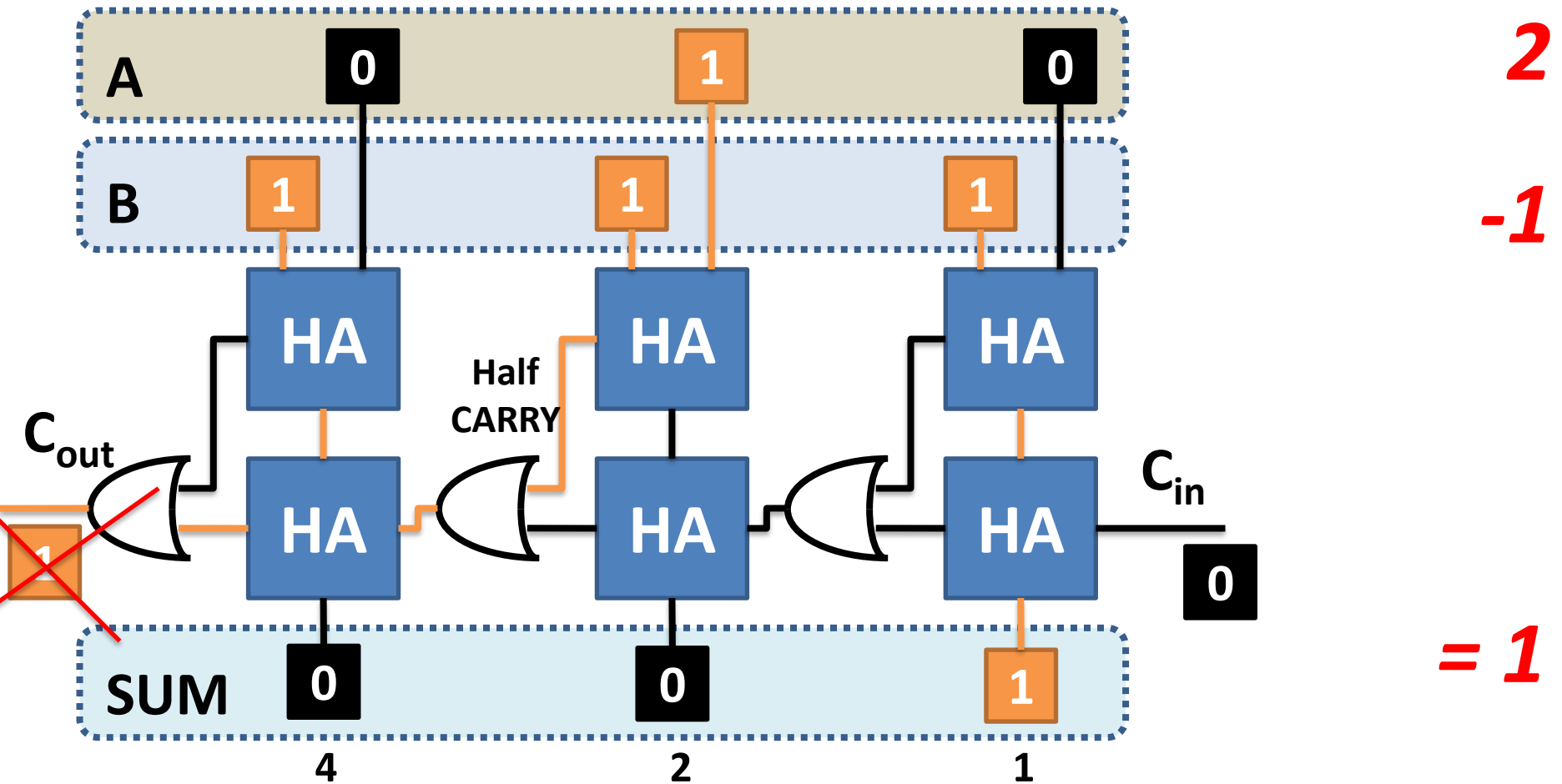


...Problem: *timing issues* – we would need to add “slow-down mechanisms”!

Carry-select adders

- Ripple-carry adders are *slow* because each stage must wait for the carry bit from the previous stage
- Solution: Split the problem: add the “lower” $n/2$ bits and the “upper” $n/2$ bits independently
 - Add the lower $n/2$ bits as normal
 - For the upper $n/2$ bits, use **two** sets of full adders: one set assumes $C_{in} = 0$, ...the other assumes $C_{in} = 1$
 - When we’ve added the first n bits, we’ll know which set to use
 - This effectively **doubles the speed**
 - And we can keep splitting as long as cost/ space allows

Carry-select adder

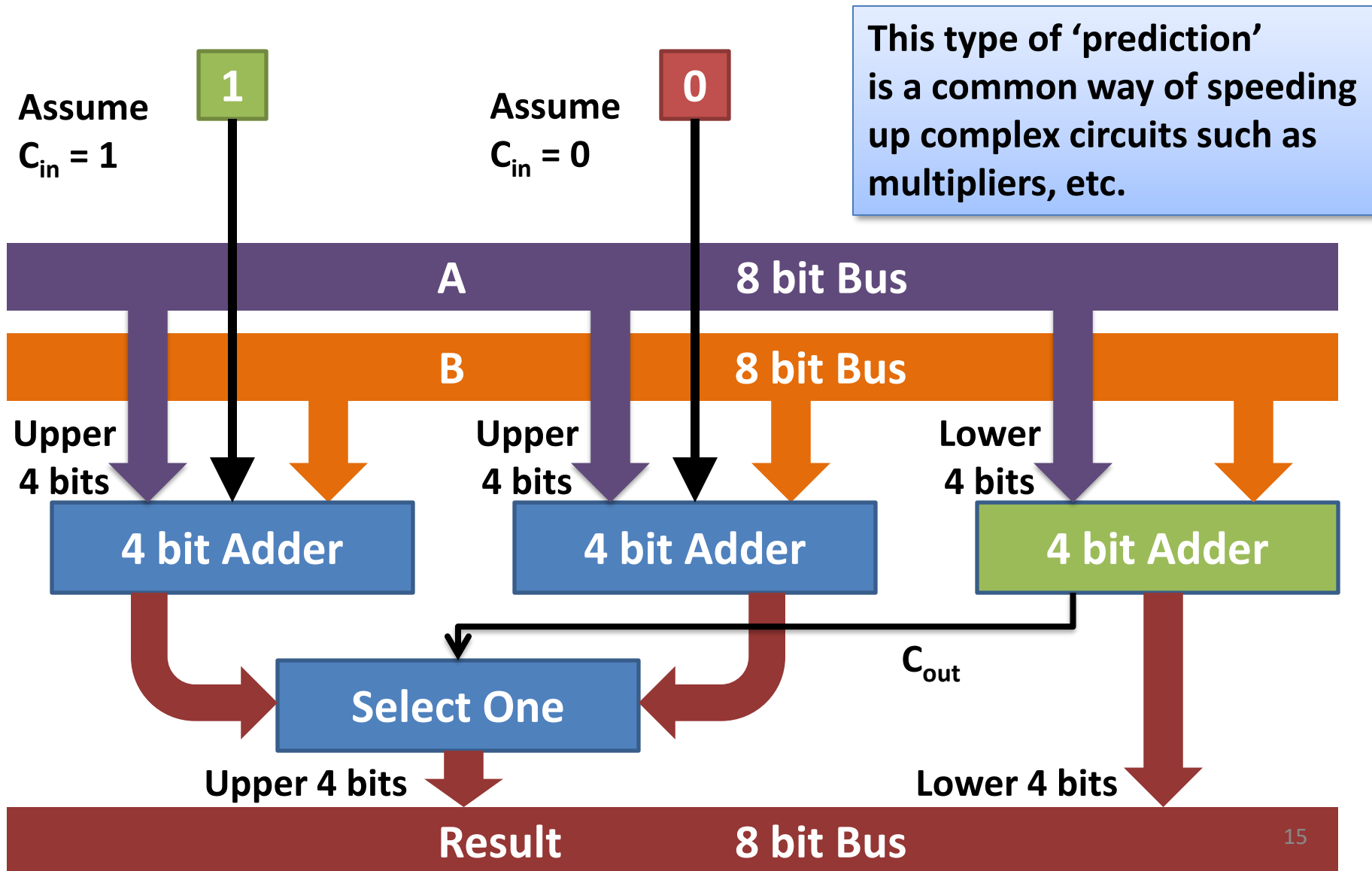

Checkpoint: how far have we got with our ALU? (1)

- We can add whole numbers
 - And, of course, **using two's complement gives us subtraction, too**
- ...and **subtraction allows us to do comparisons:**
- <, >, =
- (do “subtraction”, then check for +ve, -ve, or zero result)

Checkpoint: how far have we got with our ALU? (2)

- Multiplication and division??
 - We could do these in software, using addition and subtraction
 - Or we could do a hardware design based on long multiplication and long division methods
 - As with our adder, prediction can speed these up too


Checkpoint: how far have we got with our ALU? (3)

- Logic operations can easily be built directly from logic gates
 - AND, OR, NOT, ...

So, just the status flags to go...

The status flags

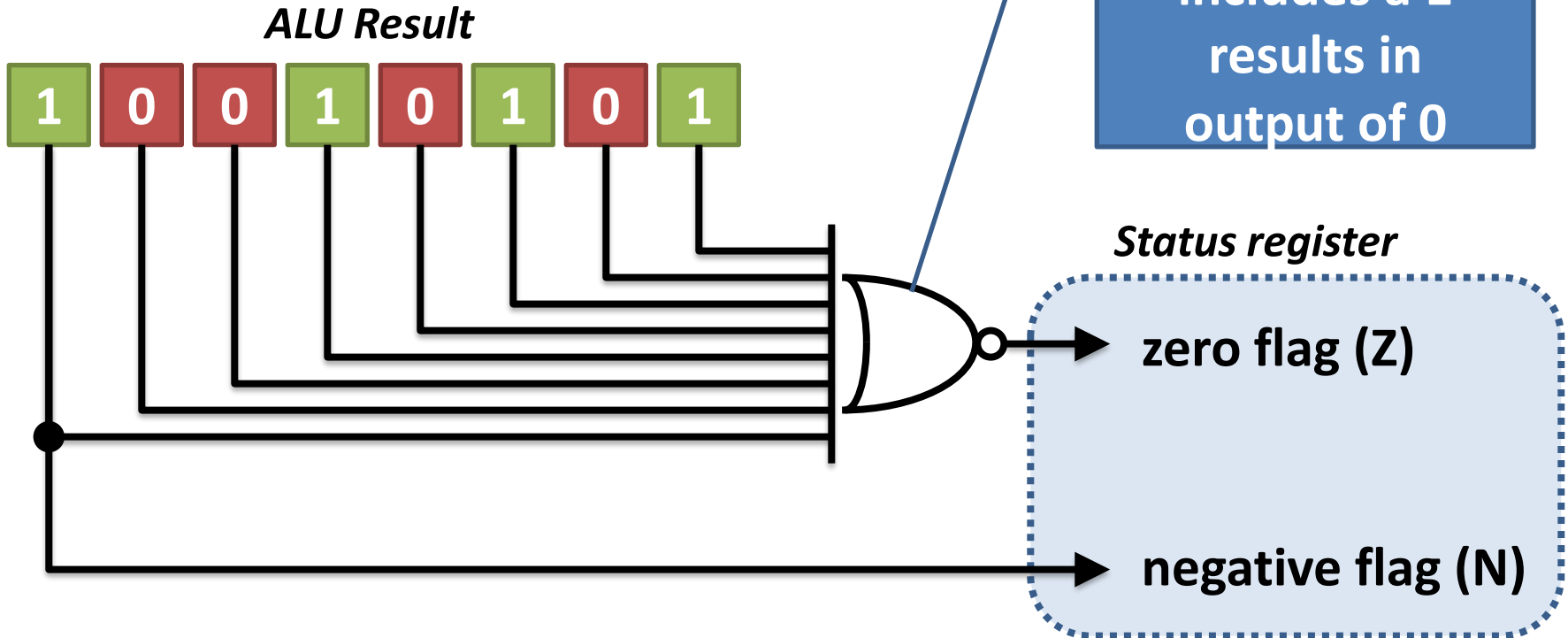- The status flags are bits organised into a special register called the *flags register*
- As we've already noted, each flag reflects an aspect of the outcome of the most recent ALU operation




The overflow flag is a little more challenging...

Overflow flag

Leftmost (sign) input bits

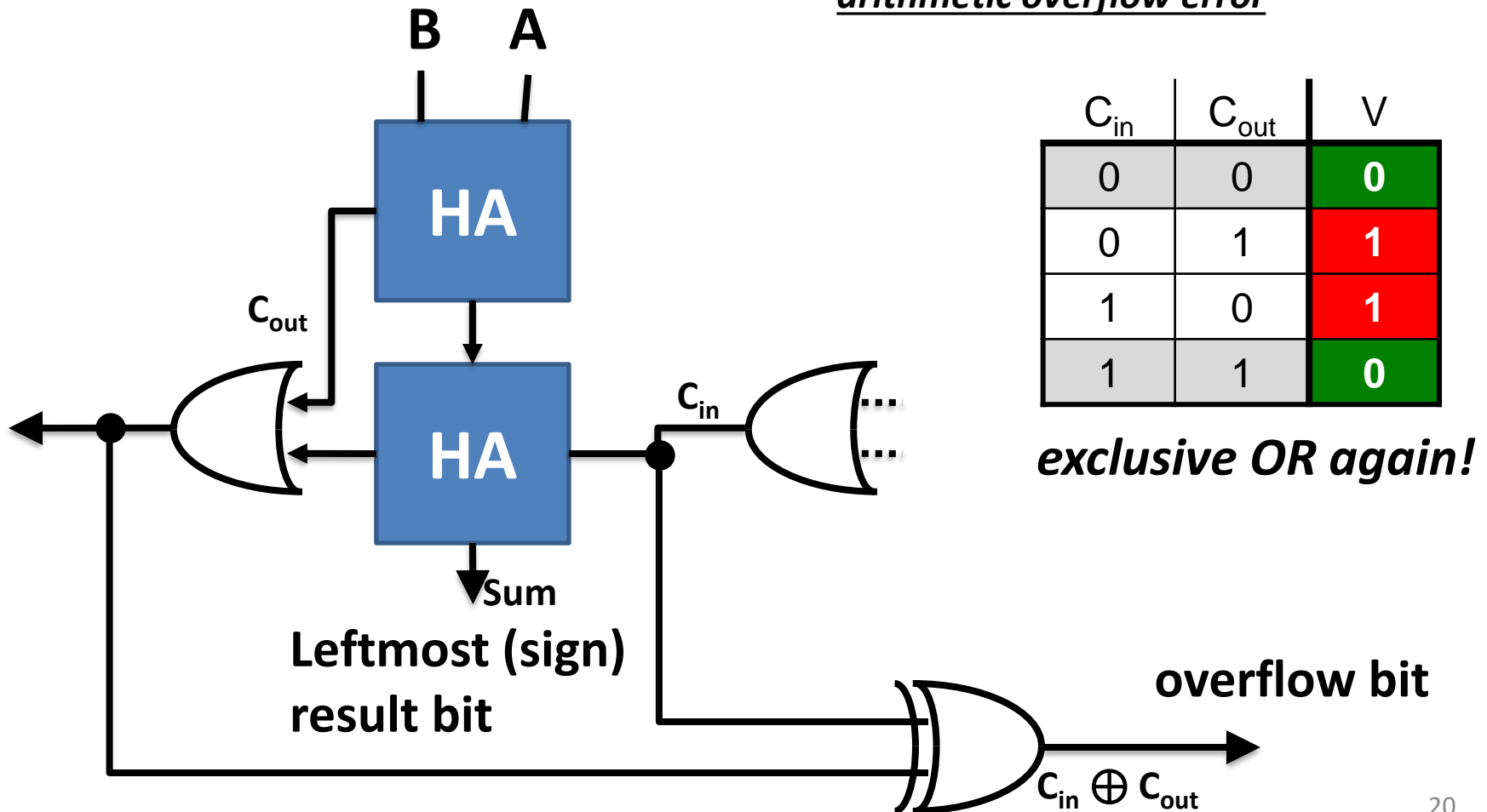“If the sign bits are the same but the result has a different sign, we have arithmetic overflow error”



Why does this work?

- If C_{in} is 0, A is 1, B is 1, SUM is 0
 - In these circumstances, we are adding two negative numbers and getting a positively-signed result
- If C_{in} is 1, A is 0, B is 0, SUM is 1
 - In these circumstances, we are adding two positive numbers and getting a negatively-signed result

In Both situations, Overflow bit:
 $C_{in} \oplus C_{out} = 1$ indicating arithmetic overflow error

1 bit addition

C_{in}	A	B	SUM	C_{out}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

“If the sign bits are the same but the result has a different sign, we have arithmetic overflow error”


Bit shifting (1)

- As we've already seen, bit shifting enables simple multiplication/ division by powers of two, and can also speed up addition-based methods of multiplication
- Movement of a bit pattern left or right is also widely used in control systems and pattern matching

Bit shifting (2)

- Mainly 4 types of shifts: ***arithmetic shift (considers 2's complement), logical shift, rotate, and rotate through carry***
- A simple “shifter” is shown on the next slide
 - More complex shifters can shift by multiple bits in a single operation (e.g. they employ “barrel shifters”)
 - (Can you design this circuit from scratch, maybe a 3-bit version, using our now-familiar approach of:
truth table → “sum of products” logic expression → logic circuit??)

Basic logical shift L/R

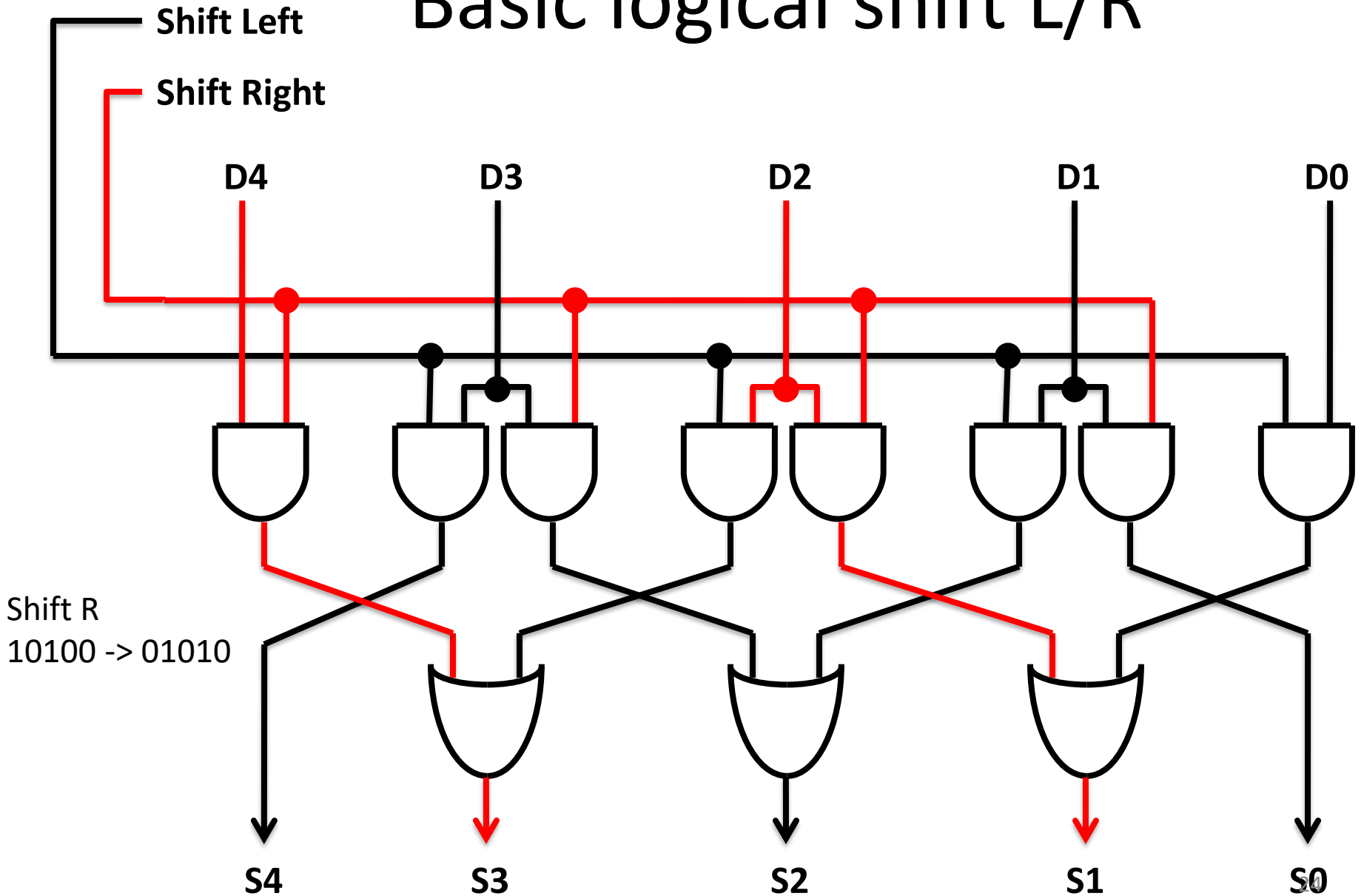

Summary

- We know (minimal forms of) all the fundamental facilities that an ALU needs to provide
 - We know how to do addition and, given 2's complement, subtraction
 - We can do this using full adders combined into either *ripple-carry* or *carry-select* multi-digit adders
 - We know how to implement the zero, negative and overflow flags
 - We know how to do bit shifting
- Again, all this is a *minimal* basis for an ALU – a real ALU will likely offer more!