

SCC131: Digital Systems

Topic 4: Boolean logic

Boolean (a.k.a. binary) logic

- The fundamental binary logical operators are **AND**, **OR**, **NOT** and **XOR**
- They are very commonly seen in programming languages:
 - e.g., conditional and looping statements in Java or C
 - `if (expression && ...) ... /* && is logical AND */`
 - `while (expression || ...) ... /* || is logical OR */`
 - etc.
 - e.g., bit manipulation in C
 - `byte1 = byte1 & 0x7f; // Clear top bit of byte (n.b. & is bitwise AND)`
 - `byte2 = byte2 | 0x80; // Set top bit of byte (n.b. | is bitwise OR)`
- But boolean logic is also crucial to the design of computer hardware at the lowest level...

Boolean logic operations can be understood as “truth tables”

- For any pair of binary digits (bits) A and B...

AND

A	B	Q
0	0	0
0	1	0
1	0	0
1	1	1

TRUE if, and only if, all inputs are TRUE

OR

A	B	Q
0	0	0
0	1	1
1	0	1
1	1	1

TRUE if any input is TRUE

NOT

A	Q
0	1
1	0

TRUE if, and only if, the single input is FALSE

XOR

A	B	Q
0	0	0
0	1	1
1	0	1
1	1	0

(eXclusive OR)

True if an odd number of inputs are TRUE, otherwise FALSE

1 is interpreted as meaning TRUE; and 0 as FALSE

Notation

- Instead of AND/OR/NOT/XOR you will often see
 - AND: \bullet or \wedge or *<nothing>*
cf. "product"
 - OR: $+$ or \vee
cf. "sum"
 - NOT: $'$ or $\bar{}$ (*bar*) or \neg
 $'$ may be pronounced as *prime*
 $\bar{}$ may be pronounced as *bar*
 - XOR: \oplus

Note also the strong relationship to set theory and set operations
*...see discrete maths course*⁴

Logic components (a.k.a. “logic gates”)

AND

A	B	Q
0	0	0
0	1	0
1	0	0
1	1	1

OR





A	B	Q
0	0	0
0	1	1
1	0	1
1	1	1

NOT

A	Q
0	1
1	0

XOR

A	B	Q
0	0	0
0	1	1
1	0	1
1	1	0

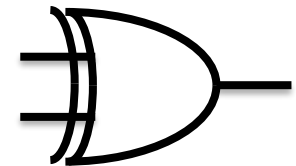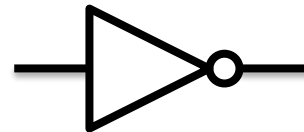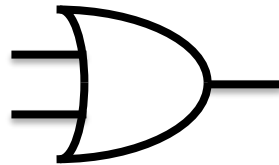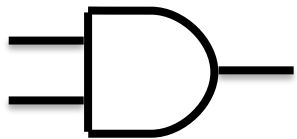


Inverted logical operations

- In practice, different gates, called NANDs and NORs, are very commonly used instead of AND/OR/NOT/XOR gates

- $A \text{ NAND } B = (A \text{ AND } B)'$


- $A \text{ NOR } B = (A \text{ OR } B)'$

- NOT AND \rightarrow **NAND**

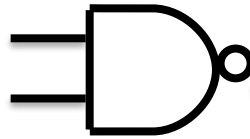

indicates inversion

- NOT OR \rightarrow **NOR**

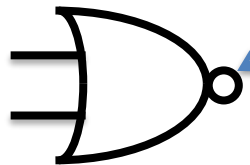

- This is because NAND and NOR are “universal”: **any** binary logic circuit can be built entirely from NAND gates, or from NOR gates
 - Also: using only NANDs (or NORs) makes circuit design significantly more cost-effective, as only one type of component is needed

NAND and NOR as truth tables...

AND

A	B	Q
0	0	0
0	1	0
1	0	0
1	1	1

OR

A	B	Q
0	0	0
0	1	1
1	0	1
1	1	1


NAND

A	B	Q
0	0	1
0	1	1
1	0	1
1	1	0


NOR

A	B	Q
0	0	1
0	1	0
1	0	0
1	1	0


Building AND/OR/NOT from NANDs/NORs

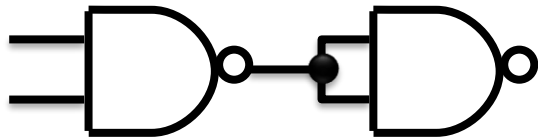


AND

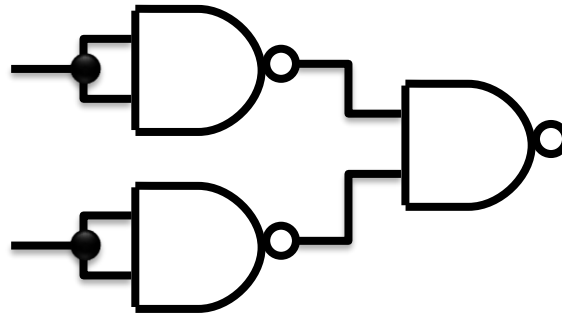


OR

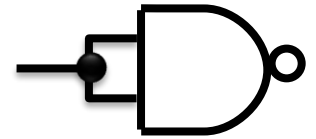


NOT

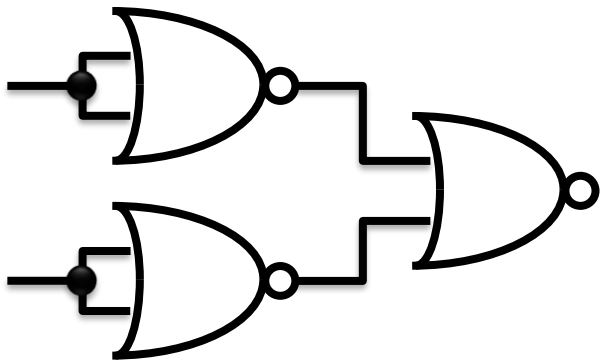

AND

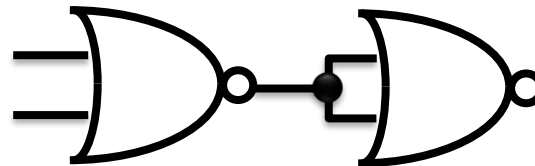


OR

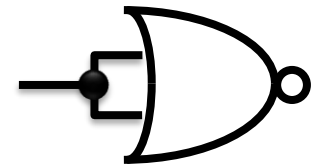

NOT

Crossing wires
(no connection)

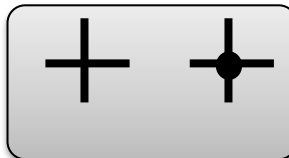

Junction
(connection)

What can we use to build computer logic?



Transistors



Vacuum Tubes



**Electro-mechanical
Relays**




Sheet Metal

...anything we can build a switch from

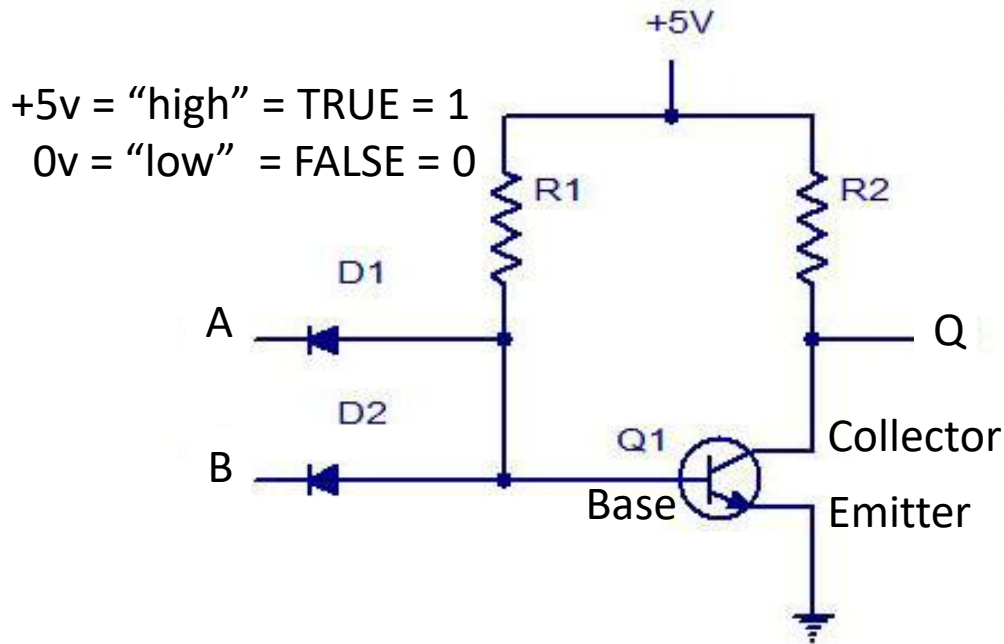Example: building a NAND gate from a transistor

- Applying +5v to inputs A and B “opens” the transistor that so current can flow from the collector to the emitter, taking Q down to 0
– (n.b. this is our sole foray into analog electronics!)



NAND		
A	B	Q
0	0	1
0	1	1
1	0	1
1	1	0

Boolean algebra

	Law	AND form	OR form
proven on next slide	Identity 1	$A = A''$	$A = A''$
	Identity 2	$1A = A$	$0 + A = A$
	Null	$0A = 0$	$1 + A = 1$
	Idempotence	$AA = A$	$A + A = A$
	Complementarity	$AA' = 0$	$A + A' = 1$
familiar from School?	Commutativity	$AB = BA$	$A + B = B + A$
	Associativity	$(AB)C = A(BC)$	$(A + B) + C = A + (B + C)$
	Distributivity	$A + BC = (A + B)(A + C)$	$A(B + C) = AB + AC$
	Absorption	$A(A + B) = A$	$A + AB = A$
	de Morgan's law	$(AB)' = A' + B'$	$(A + B)' = A'B'$

Note relationship between AND and OR variants... Swap 0s and 1s, ANDs and ORs
 ...one function is the **dual** of the other – if a function is correct, its dual must also be

Demonstration of (some of) the laws of Boolean Algebra by *perfect induction*

- That is, by tabulating all possible combinations!

Complementarity

Identity 1

$A = A''$		
A	A'	A''
0	1	0
1	0	1

Identity 2

$1A = A$		
1	A	1 AND A
1	0	0
1	1	1

Null

$0A = 0$		
0	A	0 AND A
0	0	0
0	1	0

Idempotence

$AA = A$		
A	A	A AND A
0	0	0
1	1	1

-tarity

$AA' = 0$		
A	A'	A AND A'
0	1	0
1	0	0

(OR form of Identity 1 is same as above)

$0 + A = A$		
0	A	0 OR A
0	0	0
0	1	1

$1 + A = 1$		
1	A	1 OR A
1	0	1
1	1	1

$A + A = A$		
A	A	A OR A
0	0	0
1	1	1

$A + A' = 1$		
A	A'	A OR A'
0	1	1
1	0	1

Proof of absorption by perfect induction

$A(A+B) = A$			
A	B	A + B	A (A+B)
0	0	0	0
0	1	1	0
1	0	1	1
1	1	1	1



$A + AB = A$			
A	B	AB	A + AB
0	0	0	0
0	1	0	0
1	0	0	1
1	1	1	1



de Morgan's Law

- $(AB)' = A' + B'$ $(A + B)' = A'B'$ *Very useful!*
- Whenever we see an expression whose sub-expressions are all ANDed together, or all ORed together, we can re-state by
 1. negating the overall expression
 2. negating the sub-expressions
 3. flipping the operators from OR to AND, or vice versa
- Can you demonstrate, using perfect induction (i.e. a truth table), that $(A' + B')' = AB$???

Towards the design of logic circuits

- Here are some examples of logic circuits that we might want to design
 - Traffic lights, counters, clocks, multiplexers, segmented numeric displays, ...
 - *Computer ALUs, computer control units, computer memory units, buses, etc...*
- The basic approach is
 1. Write out a truth table for the desired logical function
 2. Derive a boolean expression by ORing together all the rows whose “output column” is 1
 - This is often called the ***sum-of-products*** form (cf. arithmetic “+”)
 3. Translate the Boolean expression to logic gates
 - May need to map to AND/OR/NOT gates or to NAND or NOR only
 - May need to use Boolean algebra or “Karnaugh maps” (see later) to obtain the simplest mapping to our target types of logic gate

A first example of logic circuit design (XOR)


- Consider a *stair-hall lighting circuit* – a light over the stairs is controlled by a switch **H** in the hall, and a switch **S** on the stairs
 - We want to be able to switch the light on at the bottom, and off again at the top—and vice versa
 - So, we want the light to be on if **S** is *up* and **H** is *down*, **or** if **S** is *down* and **H** is *up*

	S	H	Light
	0	0	0
S'H	0	1	1
SH'	1	0	1
	1	1	0

Example *contd.*

- So, $L = S'H + SH'$ [*in sum-of-products form*]
- Let's implement this using NAND gates...
- Apply de Morgan's law
 - Let $X = S'H$ and let $Y = SH'$ So we have $X + Y$
 - By de Morgan's law, $X + Y = (X' Y')'$
 - Expand to $((S'H)' (SH'))'$ So $L = ((S'H)' (SH'))'$
 - This is now in the required “inverted AND” form...


Example *contd.*

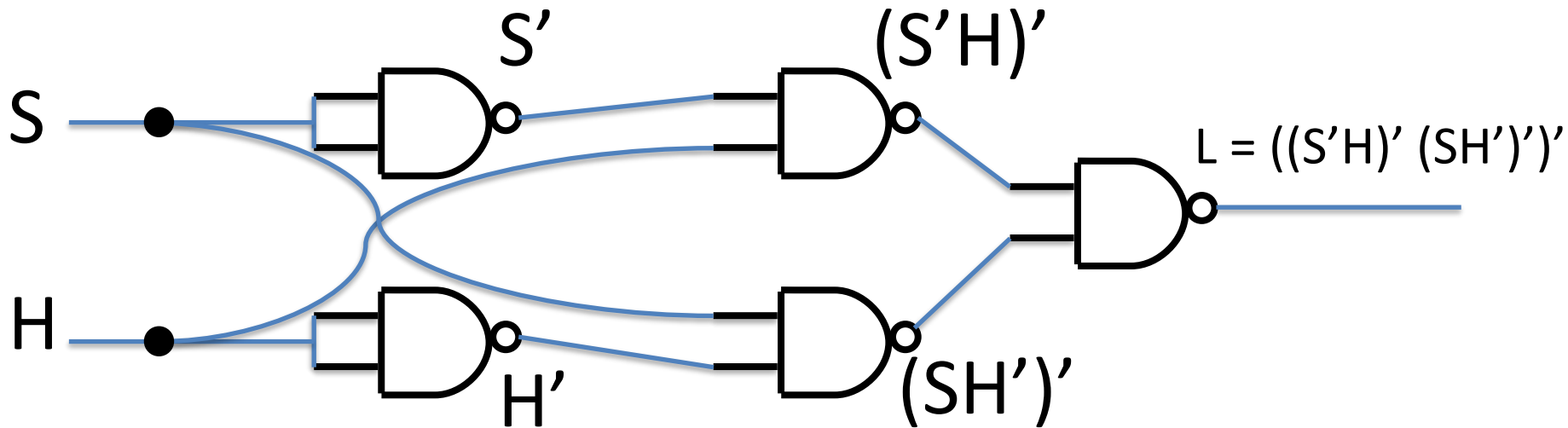

$$L = ((S'H)' (SH'))'$$

A second example: design a 4-way multiplexer

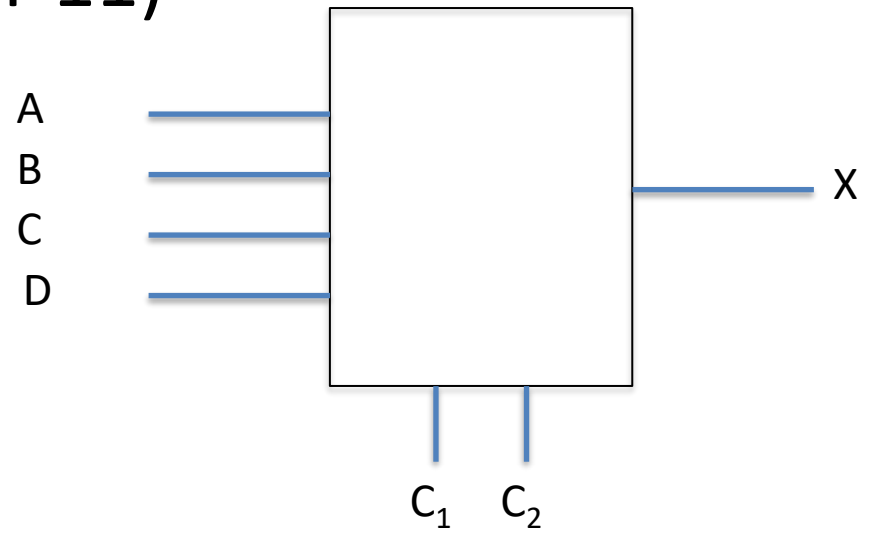- We want a multiplexer that “lets through” one of four inputs A, B, C or D, depending on the values of control inputs C_1 and C_2 (i.e. 4 control possibilities: 00, 01, 10 or 11)
 - $C_1=0$ $C_2=0$ makes $X=\mathbf{A}$
 - $C_1=0$ $C_2=1$ makes $X=\mathbf{B}$
 - $C_1=1$ $C_2=0$ makes $X=\mathbf{C}$
 - $C_1=1$ $C_2=1$ makes $X=\mathbf{D}$



Multiplexer example *cont.*

- Write out the truth table and derive the sum-of-products form:

$$X = (AC_1'C_2') + (BC_1'C_2) + (CC_1C_2') + (DC_1C_2)$$

(each term is taken from an “X=1” row)

C ₁	C ₂	A	B	C	D	X
0	0	1	X	X	X	1
0	0	0	X	X	X	0
0	1	X	1	X	X	1
0	1	X	0	X	X	0
1	0	X	X	1	X	1
1	0	X	X	0	X	0
1	1	X	X	X	1	1
1	1	X	X	X	0	0


N.B., an X in a truth table means either 0 or 1 – i.e. “don’t care”; this is useful in reducing the number of rows we have to consider!

Example *cont.*

- Apply de Morgan's law to get this into "inverted AND" form

$$\begin{aligned} & AC_1'C_2' + BC_1'C_2 + CC_1C_2' + DC_1C_2 \\ &= \\ & ((AC_1'C_2')' (BC_1'C_2)' (CC_1C_2')' (DC_1C_2)')' \end{aligned}$$

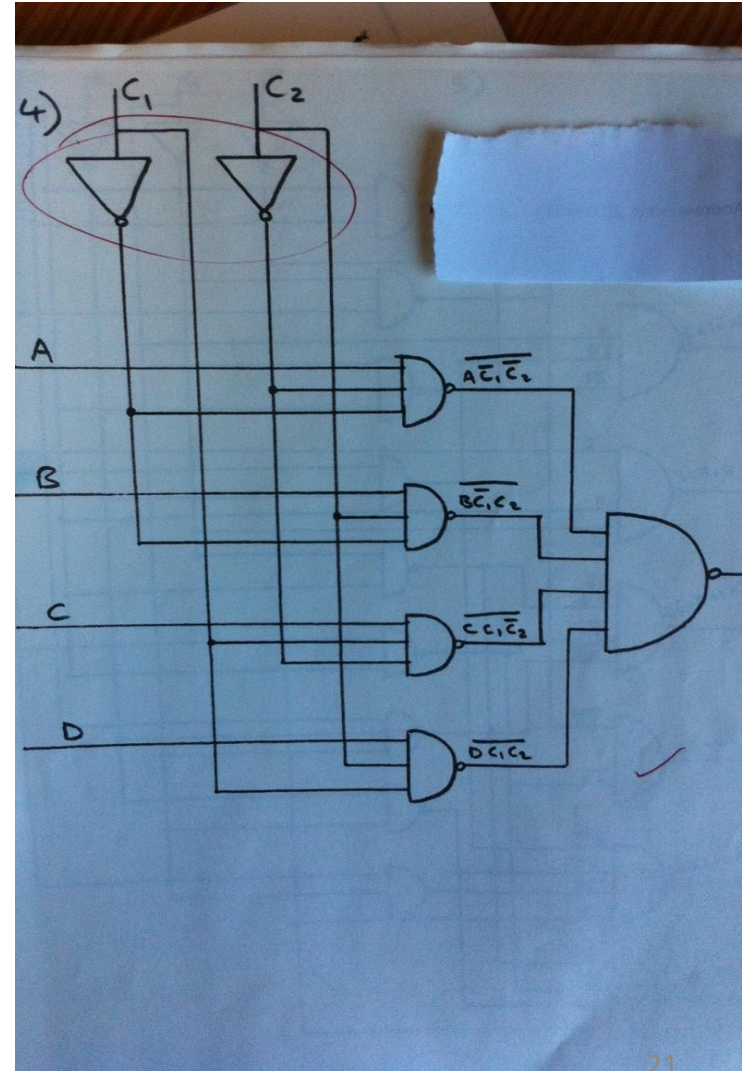- Now we can map directly to 3-input NANDs...



Using Karnaugh maps (K-map) to minimise Boolean logic functions

- Our examples so far have mapped “conveniently” to NAND gates; we have just needed de Morgan’s law to translate to “inverted AND” form
 - But it’s not always so straightforward in practice - using a truth table directly will often lead to a more complex implementation than necessary
- We can often *minimise* a Boolean function to produce a functionally equivalent, but simpler, implementation
- Karnaugh maps (K-map) offer an easy way to do this...

What is a Karnaugh map (K-map)?

- A grid in which each square represents one possible combination of inputs (cf. truth table row)
- Columns/rows are ordered so that only one input “changes” from col-to-col, and from row-to-row

(Also: note that Karnaugh maps “wrap” left-to-right and top-to-bottom)

	A	A'
B		
B'		

2-input map

	AB	A'B	A'B'	AB'
C				
C'				

3-input map

	AB	A'B	A'B'	AB'
CD				
C'D				
C'D'				
CD'				

4-input map

Using a Karnaugh map (K-map)

1. Pick a template with the required number of inputs, and put a 1 in any square for which we want an output of 1
2. Look for *rectangular groups* of 1s
 - Groups must contain 2 or 4 or 8 ... (2^n) cells
 - Groups may overlap, and may wrap around the edges
 - The *larger* the groups, and the *fewer* the groups, the better

Result: for each group simply list the “unchanged” terms and OR them together (“changed” ones “cancel”)

$$\begin{aligned}
 & \text{A'BCD} + \text{A'B'CD} + \\
 & \text{A'BC'D} + \text{A'B'C'D} + \text{AB'C'D} + \\
 & \text{ABCD'} + \text{A'BCD'} + \text{A'B'CD'} + \text{AB'CD'} \\
 & = \underline{\text{A'D}} + \underline{\text{AB'C'}} + \underline{\text{CD'}}
 \end{aligned}$$

	AB	A'B	A'B'	AB'
CD		1	1	
C'D		1	1	1
C'D'				1
CD'	1	1	1	1

Karnaugh map example

- Implement a Decoder function that detects the following inputs: 0, 1, 2, 4 and 5 (assume 3-bit binary)
- Here's the truth table:

Decimal	Binary			Output
	A	B	C	
0	0	0	0	1
1	0	0	1	1
2	0	1	0	1
3	0	1	1	0
4	1	0	0	1
5	1	0	1	1
6	1	1	0	0
7	1	1	1	0

Identify the sum-of-products expression

- $F = A'B'C' + A'B'C + A'BC' + AB'C' + AB'C$

Decimal	Binary			Output	Term
	A	B	C		
0	0	0	0	1	$A'B'C'$
1	0	0	1	1	$A'B'C$
2	0	1	0	1	$A'BC'$
3	0	1	1	0	
4	1	0	0	1	$AB'C'$
5	1	0	1	1	$AB'C$
6	1	1	0	0	
7	1	1	1	0	

Now, enter these five terms into a 3-input Karnaugh map template...

- $F = A'B'C' + A'B'C + A'BC' + AB'C' + AB'C$

	AB	A'B	A'B'	AB'
C	0	0	1	1
C'	0	1	1	1

Find the groups

- $F = A'B'C' + A'B'C + A'BC' + AB'C' + AB'C$

	AB	A'B	A'B'	AB'
C			1	1
C'		1	1	1

The **larger** the groups the better
The **fewer** the groups the better...
(doesn't matter if groups overlap)

Derive the result...

- Look for the “unchanged” variables in each group

B' is unchanged (“A” cancels: appears as both A and A'; “C” cancels: appears as both C and C')

	AB	A'B	A'B'	AB'
C			1	1
C'		1	1	1

A'C' is unchanged (“B” cancels: appears as both B and B')

Result

- Write down and OR together the “unchanged” variables...
 - **B'** was unchanged
 - **A'C'** was unchanged
- Result is therefore, **$F = B' + A'C'$**
- (Can you derive an implementation using NAND gates?
hint: apply de Morgan's law to our result...)
- (Can you prove that $A'B'C' + A'B'C + A'BC' + AB'C' + AB'C = B' + A'C'$ using perfect induction?)

Be careful not to miss “wrap around” possibilities

- Remember that groups may “wrap around”
- So, in each of the following examples we have a single group of four cells

	AB	A'B	A'B'	AB'
CD				
C'D	1			1
C'D'	1			1
CD'				

A and C' are “unchanged”

	AB	A'B	A'B'	AB'
CD	1			1
C'D				
C'D'				
CD'	1			1

A and C are “unchanged”

Let's do the same using Boolean algebra

- $F = A'B'C' + A'B'C + A'BC' + AB'C' + AB'C$
 - Can use *idempotence* to expand:
$$= A'B'C' + A'B'C + A'BC' + A'B'C' + AB'C' + AB'C$$
 - Can then use *distributivity* to combine “similar” pairs of terms:
$$= A'B'(C' + C) + A'(B + B')C' + AB'(C' + C)$$
 - Can then use *complementarity* and then *identity-2* to simplify:
$$= A'B' + A'C' + AB' \quad [X+X'=1 \text{ and then } 1X=X]$$
 - Can then use *commutativity* to rearrange:
$$= A'B' + AB' + A'C'$$
 - Can then use *distributivity* (again):
$$= (A' + A)B' + A'C'$$
 - Can then use *complementarity* and then *identity-2* (again) to simplify:
$$= B' + A'C'$$


Why do Karnaugh maps “work”?

- A Karnaugh map is simply a visual representation of a logical expression in sum-of-products form
- As we just saw, we can often simplify a sum-of-products expression like this:
$$AB + AB' \Rightarrow A(B + B') \Rightarrow A$$

[via distributivity=>complementarity=>identity-2]
- This is what we informally called « cancelling »
- This is essentially what a Karnaugh map does – e.g., the fact that the **red group** below includes both B and B' allows the B variable to be cancelled from the expression

$AB + AB' =$

	A	A'
B	1	
B'	1	

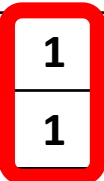 $= A$

Summary

- We know the four basic Boolean operators, and the corresponding logic gates
- We understand truth tables
- We appreciate the universality of NAND and NOR
- We understand the laws of Boolean algebra
- We promise to remember at least some of them (especially, de Morgan's law)!
- We know how to go through the following process
 - a logic function specification \rightarrow a truth table \rightarrow a “sum of products” logic expression \rightarrow a logic circuit
- We know how to minimise logic expressions using Karnaugh maps